
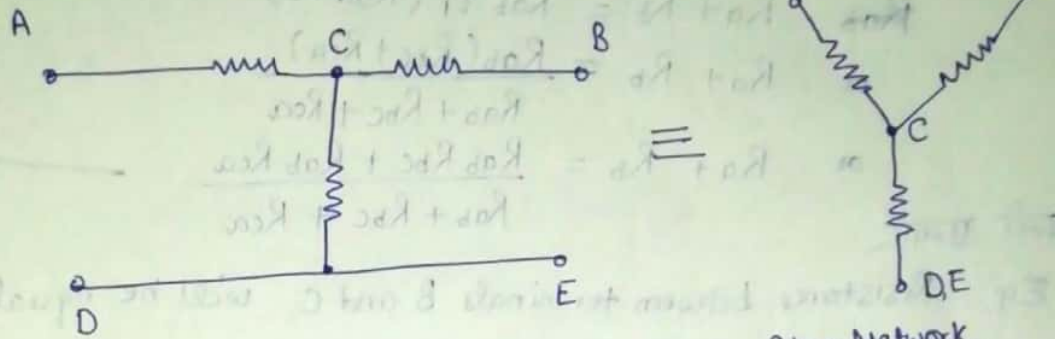
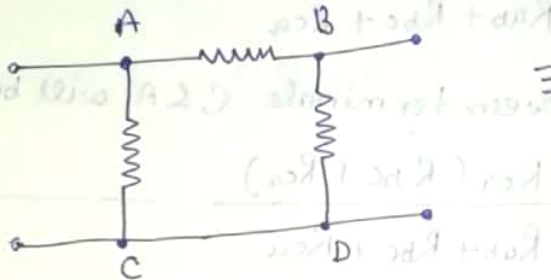
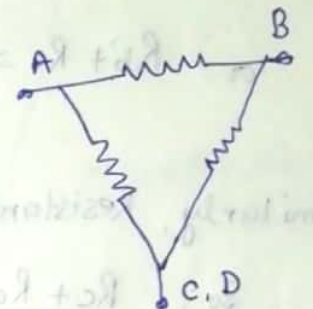
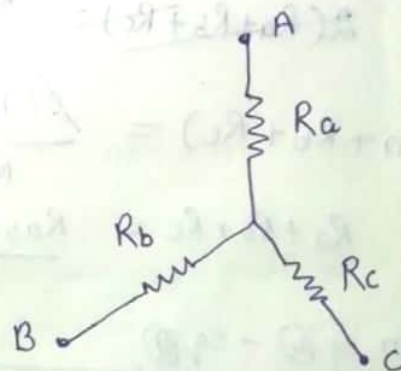


Star-Delta Transformation (स्तर-डेल्टा रूपांतरण)

T to π Conversion and π to T conversion

(a) T-Network(a) Star-Network π -network Δ -network

Delta to Star Conversion

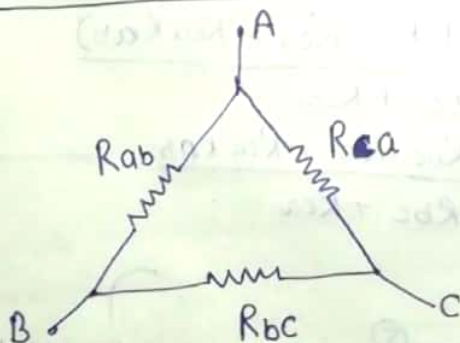

दो network (star or Delta) तभी equivalent होंगे जबकि किसी दो common terminals जैसे A तथा B, B तथा C तथा C तथा A के बीच equivalent resistance बराबर हो।

For Δ to Λ conversion,

Resistance between A & B terminals in star = Resistance between A & B terminals in Δ network.

So, $R_{ab} = R_a + R_b$

$$R_a + R_b = R_{ab} \parallel (R_{bc} + R_{ca})$$

$$\text{or } R_a + R_b = \frac{R_{ab}(R_{bc} + R_{ca})}{R_{ab} + R_{bc} + R_{ca}}$$

$$\text{or } R_a + R_b = \frac{R_{ab} R_{bc} + R_{ab} R_{ca}}{R_{ab} + R_{bc} + R_{ca}} \quad \text{--- (1)}$$

इसी प्रकार

Eq. Resistance between terminals B and C will be equal

So $R_b + R_c = \frac{R_{bc}(R_{ca} + R_{ab})}{R_{bc} + R_{ca} + R_{ab}}$

$$\text{or } R_b + R_c = \frac{R_{bc} R_{ca} + R_{bc} R_{ab}}{R_{ab} + R_{bc} + R_{ca}} \quad \text{--- (2)}$$

Similarly, Resistance between terminals C & A will be equal.

So, $R_c + R_a = \frac{R_{ca}(R_{bc} + R_{ab})}{R_{ab} + R_{bc} + R_{ca}} \quad \text{--- (3)}$

Adding eq 1, 2, and 3, we get

$$2(R_a + R_b + R_c) = \frac{2(R_{ab} R_{bc} + R_{bc} R_{ca} + R_{ca} R_{ab})}{R_{ab} + R_{bc} + R_{ca}}$$

$$R_a + R_b + R_c = \frac{R_{ab} R_{bc} + R_{bc} R_{ca} + R_{ca} R_{ab}}{R_{ab} + R_{bc} + R_{ca}} \quad \text{--- (4)}$$

from eq (4) - eq (1),

$$R_a = \frac{R_{ab} R_{ca}}{R_{ab} + R_{bc} + R_{ca}} \quad \text{--- (5)}$$

from eq (4) - eq (2),

$$R_b = \frac{R_{bc} R_{ab}}{R_{ab} + R_{bc} + R_{ca}} \quad \text{--- (6)}$$

Similarly eq (4) - eq (3),

$$R_c = \frac{R_{ca} R_{bc}}{R_{ab} + R_{bc} + R_{ca}} \quad \text{--- (7)}$$

used for
 Δ to Λ
conversion

For Δ to Δ conversion
from eq (5), (6) and (7),

$$R_a R_b + R_b R_c + R_c R_a = \frac{R_a^2 R_b R_c R_c}{(R_a + R_b + R_c)^2} + \frac{R_a R_b R_c^2 R_c}{(R_a + R_b + R_c)^2} + \frac{R_a R_b R_c R_c^2}{(R_a + R_b + R_c)^2}$$

$$\text{or } R_a R_b + R_b R_c + R_c R_a = \frac{R_a^2 R_b R_c R_c + R_a R_b R_c^2 R_c + R_a R_b R_c R_c^2}{(R_a + R_b + R_c)^2}$$

$$\text{or } R_a R_b + R_b R_c + R_c R_a = \frac{R_a R_b R_c R_c (R_a + R_b + R_c)}{(R_a + R_b + R_c)^2}$$

$$\text{or } R_a R_b + R_b R_c + R_c R_a = \frac{R_a R_b R_c R_c}{R_a + R_b + R_c} \quad \text{--- (8)}$$

from eq (8) $\div$ eq (7)

$$\frac{R_a R_b + R_b R_c + R_c R_a}{R_c} = R_a$$

$$\text{or } R_a = \frac{R_a R_b}{R_c} + R_a + R_b$$

Used for Δ to Δ conversion

Similarly from, eq (8) $\div$ eq (5),

$$R_b = R_b + R_c + \frac{R_b R_c}{R_a}$$

and

$$R_c = R_c + R_a + \frac{R_c R_a}{R_b}$$